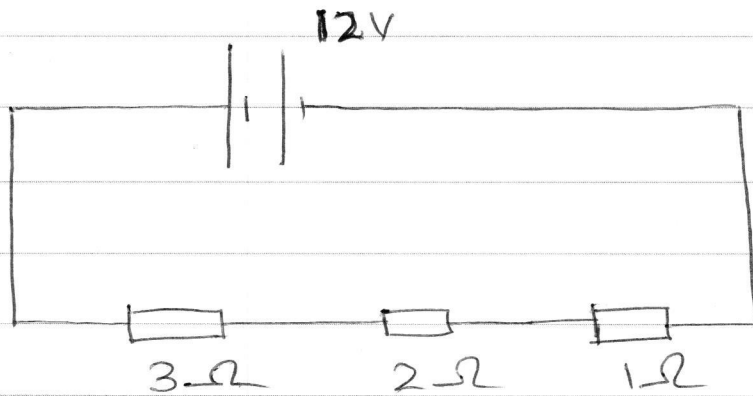



Circuit Analysis

①




Work out the current flowing through the 3Ω resistor.

②

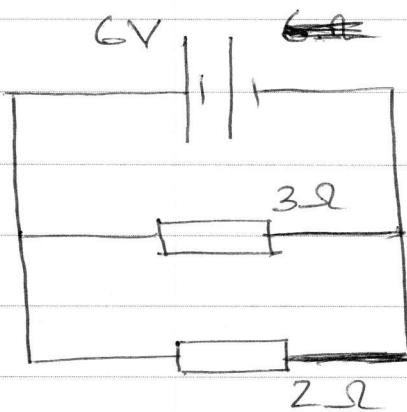

Work out the current flowing through the 3Ω resistor.

③

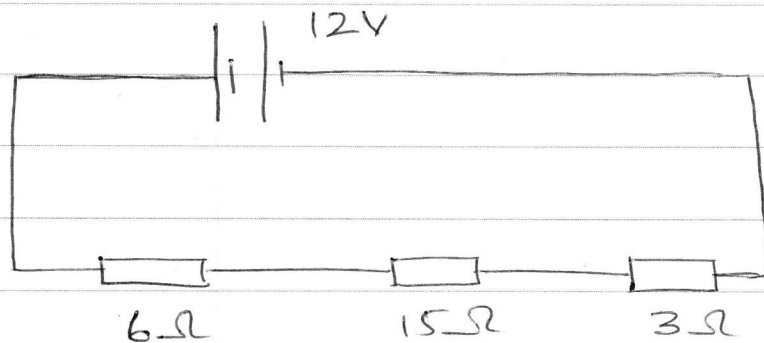

Calculate the voltage across the 15Ω resistor.