

- (c) Work out the current through the $6\ \Omega$ resistor.
- (d) Work out the current through the $2\ \Omega$ resistor.
- (e) Work out the power dissipated in the $2.5\ \Omega$ resistor.
- (f) Work out the energy supplied by the battery in 2 minutes.