

1.

(a)(i)	Ammeter		B1
(ii)	Voltmeter		B1
(b)	I : current		B1
	Δt : time (interval / duration)		B1
(c)(i)	$I = 7.5 \times 10^3 / 1500$ $I = 5.0$ (A)		C1 A1
(ii)	$V = P / I$ $V = 1.2 \times 10^3 / 5.0$ $V = 240$ (V)	(allow other variants) (possible e.c.f) (-1 for missing k or 10^3 factor)	C1 C1 A1
(iii)	$E = 1.2 \times 10^3 \times 1500$ $E = 1.80 \times 10^6$ (J)	(-1 for missing k or 10^3 factor) penalise once only in (ii) & (iii)	C1 A1
(iv)	units = $1500/3600 \times 1.2 = 0.5$ cost = $0.5 \times 6.4 = 3.2$ (p)	units = $1.8 \times 10^6 / 3.6 \times 10^6 = 0.5$ (possible (e.c.f if (iii) used)	C1 A1

2.

(a)(i)	Coulomb / C	(Allow Ampere second / As)	B1
(ii)	Voltmeter		B1
(b)(i)	$P = VI$ $V = 36 / 3.0$ p.d. = 12 (V)	(Allow other variant)	C1 C1 A1
(ii)	$E = 36 \times 600$ energy = $2.1(6) \times 10^4$ (J) $\approx 2.2 \times 10^4$ (J)		C1 A1
(iii)	$\Delta Q = I\Delta t / Q = It$ $\Delta Q = 3.0 \times 600$ charge = 1.8×10^3 (C)	(Allow other variant)	C1 C1 A1
(iv)	$N = 1.8 \times 10^3 / 1.6 \times 10^{-19}$ number = $1.1(3) \times 10^{22} \approx 1.1 \times 10^{22}$	(Possible ECF)	C1 A1

3.

(a)	$R = V / I$ symbols defined: R = resistance, V = p.d. / voltage and I = current ($V = IR$ with all symbols defined scores 1/ 2) (R = p.d. / voltage per unit current scores 2/2) (R = p.d. / voltage per unit amp / A scores 1/ 2)	C1 A1
(b)	Resistance decreases as temperature increases. Correct <u>curve</u> with R decreasing as temperature increases.	B1 B1
(c)(i)	Resistance increases (as V increases) Temperature increases / atoms vibrate more / more electron collisions (with atoms)	B1 B1
(ii)	1. $P = 24 \times 2$ $P = 48$ (W) 2. $V = 12$ (V) when current is 2.0 (A) (Allow $V = 11.0$ V from graph) $R = 12 / 2.0 = 6.0$ (Ω) 3. $R_T = 6.0 + 5.0 = 11.0$ (Ω) (possible e.c.f) 4. $V_L = 11.0 \times 2.0 = 22$ (V) $R_{circuit} = 48 / 2.0^2 = 12$ (Ω) $r = (24-22) / 2.0 = 1.0$ (Ω) $r = 12.0 - 11.0 = 1.0$ (Ω)	C1 A1 C1 A1 B1 C1 A1

4.

(a)	$\rho = RA / L$ Symbols defined: ρ = resistivity, A = <u>cross-sectional</u> area, R = resistance and L = length ($R = \rho L / A$ with all symbols defined scores 1/ 2)	M1 A1
(b)(i)	$A = \rho L / R$ $A = 4.3 \times 10^{-6} \times 1.2 \times 10^2 / 5.0$ (-1 for using L as 2.0 mm) $A = 1.0(3) \times 10^{-8}$ (m^2)	C1 C1 A1
(ii)	$t = 1.0(3) \times 10^{-8} / 2.0 \times 10^{-3}$ $t = 5.1(6) \times 10^{-6}$ (m) (possible e.c.f)	B1

5.

(a)(i)	$R = 50 \Omega$ $I = 3.0 / 50$ current = 0.06 (A)	C1 C1 A1
(ii)	$P = VI / V^2 / R / I^2 R$ power = 3.0×0.06 power = 0.18 (W) (Possible ECF)	C1 A1
(b)(i)	'Constant' <u>temperature</u> implied (wtte) (Do not allow reference to Ohm's law or to 'heating')	B1

- | | | | |
|------|----|---|----|
| (ii) | 1. | $40 \text{ } (\Omega)$ | B1 |
| | 2. | $A = \pi \times (1.0 \times 10^{-5})^2 = 3.1(4) \times 10^{-10} \text{ (m}^2\text{)}$ | B1 |
| | | $R = \rho L/A$ (Allow other variant) | C1 |
| | | $40 = 5.4 \times 10^{-8} \times L / 3.1 (4) \times 10^{-10}$ (Possible ECF) | C1 |
| | | $L = 0.23(3) \text{ (m)} \approx 0.23 \text{ (m)}$ | A1 |
| | | Length is 9too) long, therefore must be coiled (wtte) | B1 |
-

6.

- | | | |
|-------|---|----|
| (i) | $R = 1.28 / 0.80$ | C1 |
| | resistance = $1.6(0) \text{ } (\Omega)$ | A1 |
| (ii) | $R = R_1 + R_2 / 1.60 = r + 1.10 / r = (1.28 - 0.8 \times 1.1) / 0.8$ | C1 |
| | $r = 0.5(0) \text{ } (\Omega) \approx 0.5 \text{ } (\Omega)$ (Possible ECF) | A1 |
| (iii) | $p.d = 1.10 \times 0.80 = 0.88 \text{ (V)}$ (Possible ECF) | B1 |
-

7.

- | | | |
|--------|--|----|
| (a) | $\rho = RA / L$ (Allow $R = \rho/A$) | M1 |
| | Symbols defined: | |
| | (ρ = resistivity) $A =$ <u>cross-sectional area</u> , $R =$ resistance and $L =$ length | A1 |
| | (resistivity = product of resistance and cross sectional area per (unit) length
scores 2/2) | |
| | (resistivity = product of resistance and cross sectional area per (unit) metre
scores 1/2) | |
| (b)(i) | $h = 1.2 \times 10^{-5} / 3.0 \times 10^{-4}$ | C1 |
| | $h = 4.0 \times 10^{-2} \text{ (m)}$ | A0 |
| (ii) | $R = \rho/A$ | |
| | $R = 6.9 \times 10^{-2} \times 4.0 \times 10^{-2} / 3.0 \times 10^{-4}$ (-1 for 10^n error) | C1 |
| | $R = 9.2(0) \text{ } (\Omega)$ | A1 |
| | ($R = 920 \text{ } (\Omega)$ scores 1/2) | |
| (c) | Resistance decreases | M1 |
| | by a factor of four because the length is halved (and area is doubled) | A1 |
| | (Numerical approach with $R = 2.3 \text{ } (\Omega)$ scores 2/2) | |
-

8.

(a)(i)	Parallel		B1
(ii)	$R = R_1 R_2 / R_1 + R_2$ / $1/R_T = 1/R_1 + 1/R_2$		C1
	$R = 1.5 \times 1.0 / (1.5 + 1.0)$ / $R = 1/1.67$ / $1/R = 1.67$		C1
	$R = 0.6 (\Omega)$		A0
(b)(i)	e.m.f. is the (total) energy (gained) / work done <u>per</u> (unit) charge		B1
	Energy transformed into electrical / gained by charges		B1
	OR		
	$E = W/Q$		M1
	($E = \text{e.m.f.}$) $W = \text{energy gained / converted to electrical and } Q = \text{charge}$		A1
(ii)	The chemicals (within the cell)		B1
(iii)	$R = R_1 + R_2$ / $R = 0.8 + 0.6$	C1	
	$R = 1.4 (\Omega)$		A1
(iv)	$I = 1.5 / 1.4$		C1
	$I = 1.0(7) \text{ (A)}$ (Possible e.c.f)		A1
(v) 1.	$P = VI$ / $I^2 R$ / V^2/R		B1
2.	$P_{\text{int}} = 1.0(7)^2 \times 0.8 = (0.916 \text{ W})$ / $P_{\text{ext}} = 1.0(7)^2 \times 0.6 = (0.687 \text{ W})$		C1
	ratio = $0.8 / 0.6$ / ratio = $0.916/0.687$		C1
	ratio = 1.3(3)		A1
	(ratio = $0.6/0.8 = 0.75$ scores 2/3)		
	(ratio = 0.571, when $R = 1.4\Omega$ is used instead of 0.6Ω , scores 2/3)		
	(ratio = $(1.07 \times 0.8) / (1.07 \times 0.6)$ scores 0/3)		