

Capacitors 2

1.

(a) Define *capacitance*.

.....
 [1]

(b) Fig. 1.1 shows a circuit consisting of a resistor and a capacitor of capacitance $4.5\mu\text{F}$.

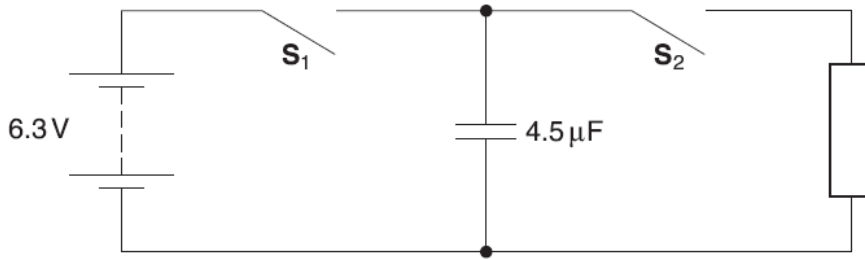


Fig. 1.1

Switch S_1 is closed and switch S_2 is left open. The potential difference across the capacitor is 6.3V .

Calculate

(i) the charge stored by the capacitor

charge = μC [1]

(ii) the energy stored by the capacitor.

energy = J [2]

(c) Switch S_1 is opened and switch S_2 is closed.

(i) Describe and explain in terms of the movement of electrons how the potential difference across the capacitor changes.

.....

 [3]

(ii) The energy stored in the capacitor decreases to zero. State where the initial energy stored in the capacitor is dissipated.

.....
 [1]

(d) Fig.1.2 shows the $4.5\mu\text{F}$ capacitor now connected in parallel with a capacitor of capacitance $1.5\mu\text{F}$. Both switches are open and both capacitors are uncharged.

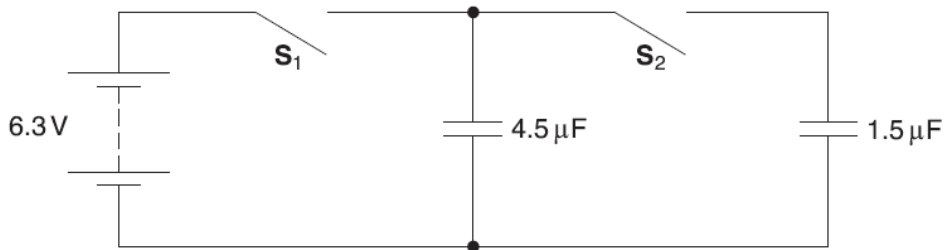


Fig. 1.2

Switch S_1 is closed. The potential difference across the $4.5\mu\text{F}$ capacitor is now 6.3V. Switch S_1 is opened and then switch S_2 is closed.

(i) Calculate the total capacitance of the circuit when S_2 is closed.

capacitance = μF [1]

(ii) Calculate the final potential difference across the capacitors.

potential difference = V [2]

2.

(a) Define *capacitance*.

.....
..... [1]

(b) Fig. 2.1 shows two capacitors of capacitance $150\ \mu\text{F}$ and $450\ \mu\text{F}$ connected in series with a battery of e.m.f. 6.0V . The battery has negligible internal resistance.

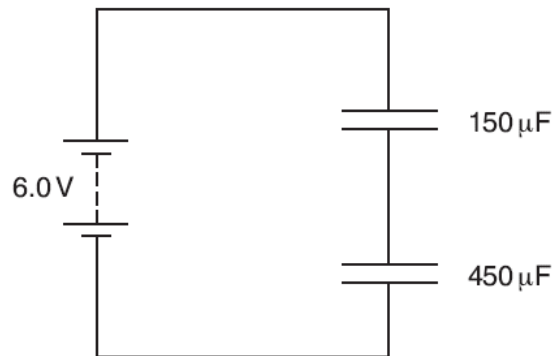


Fig. 2.1

For the circuit shown in Fig. 2.1, calculate

(i) the potential difference across the $150\ \mu\text{F}$ capacitor

potential difference = V [2]

(ii) the charge stored by the $150\ \mu\text{F}$ capacitor

charge = C [1]

(iii) the total capacitance of the circuit.

capacitance = F [1]

- (c) The fully charged capacitors shown in (b) are disconnected from the battery. The capacitors are then connected in series with a resistor R of resistance $45\text{k}\Omega$ and an open switch S as shown in Fig. 2.2.

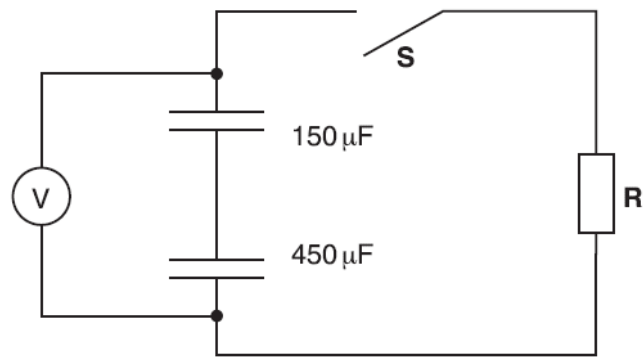


Fig. 2.2

The p.d. V across the capacitors is measured with a voltmeter of infinite resistance. The switch S is closed at time $t = 0$ and measurements of V are made at regular time intervals.

- (i) Show that the time constant for the circuit is about 5 s.

[1]

- (ii) On Fig. 2.3 sketch the variation of p.d. V with time t .

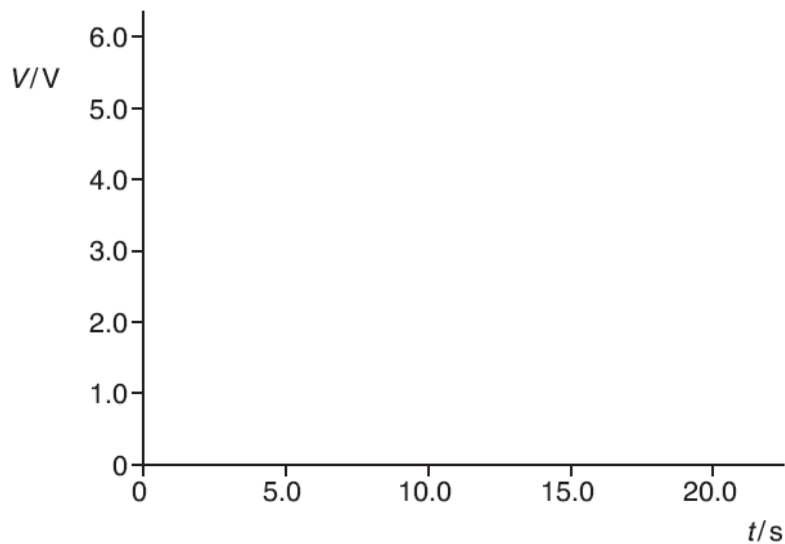


Fig. 2.3

[3]

(iii) At time $t = 0$ calculate the ratio

$$\frac{\text{energy stored by the } 150\ \mu\text{F capacitor}}{\text{energy stored by the } 450\ \mu\text{F capacitor}}$$

ratio = [2]

(iv) State and explain how the ratio varies with time.

.....
.....
..... [2]

3.

(a) Define *capacitance*.

.....
..... [1]

(b) Fig. 4.1 shows an arrangement of three identical capacitors connected to a 6.0V battery.

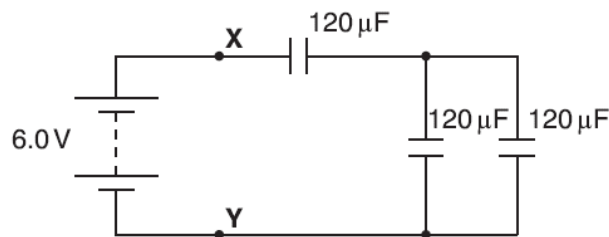


Fig. 4.1

Each capacitor has a capacitance of $120\ \mu\text{F}$.

(i) Show that the total capacitance of the circuit is $80\ \mu\text{F}$.

[2]

(ii) Calculate the total energy stored by the capacitors.

energy = J [2]

(iii) The battery is disconnected from the circuit shown in Fig. 4.1. The p.d. between points X and Y remains at 6.0V. A fixed resistor of resistance R is now connected between X and Y. Fig. 4.2 shows the variation of the p.d. V across the resistor with time t .

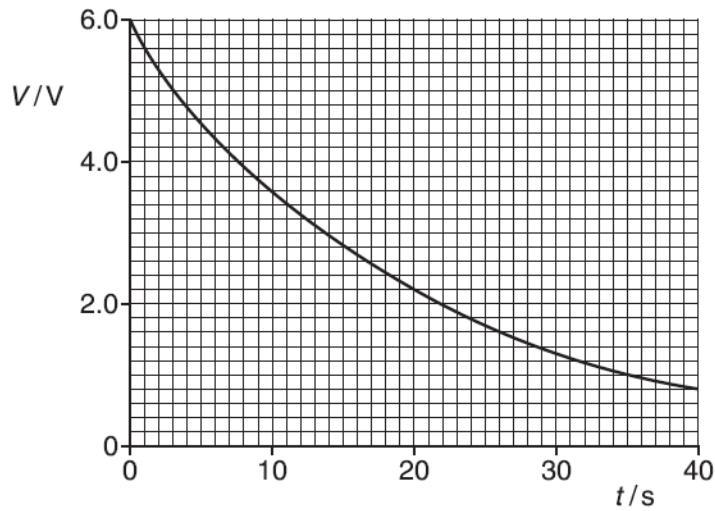


Fig. 4.2

1 Use Fig. 4.2 to show that the circuit has a time constant of 20s.

[1]

2 Hence, calculate the resistance R of the resistor.

$R = \dots \Omega$ [2]

4.

This question is about charging and discharging a capacitor.

Fig. 4.1 shows a circuit, consisting of two resistors, a capacitor and two milliammeters A_1 and A_2 , which can be connected to a 12V supply through a switch S . Initially, the switch S is open and the capacitor is uncharged.

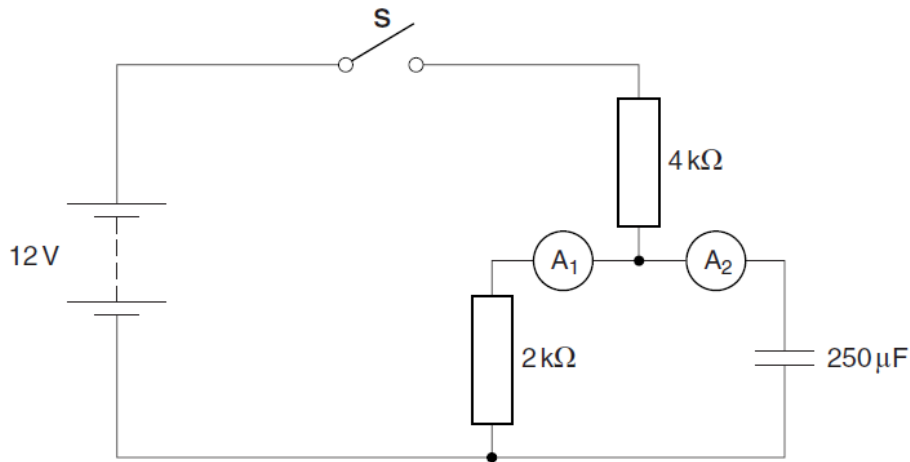


Fig. 4.1

(a) When the switch S is closed, explain why the initial current readings are

(i) zero on A_1

.....
..... [2]

(ii) 3.0 mA on A_2 .

.....
.....
..... [2]

(b) After the capacitor has fully charged

(i) state the readings of

1 ammeter A_1 mA [1]

2 ammeter A_2 mA [1]

(ii) explain why the voltage across the capacitor is 4.0V

.....
.....
..... [2]

(iii) calculate the charge Q stored on the capacitor.

$Q = \dots\dots\dots$ C [2]

(c) The switch **S** is now opened.

(i) State the initial reading of ammeters A_1 and A_2 .

..... mA [1]

(ii) Calculate the value of the time constant for the decay of charge on the capacitor.

time constant = s [1]

(iii) Plot a graph on the axes of Fig. 4.2 of the reading I of ammeter A_2 from $t = 0$, when the switch is opened, to $t = 1.5$ s. Label the y-axis with a suitable scale. [3]

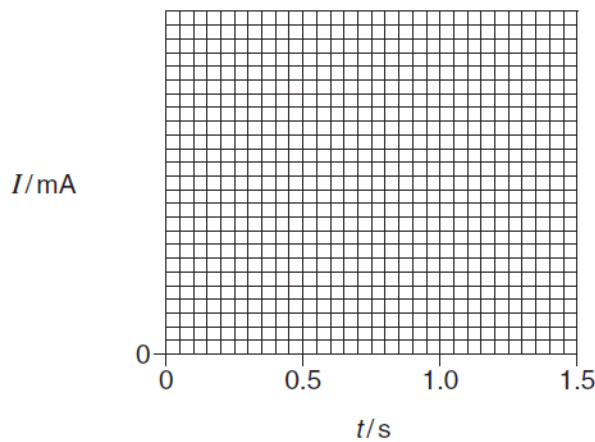


Fig. 4.2