

Electricity 2

1. Fig.1 shows a lamp connected to a battery.


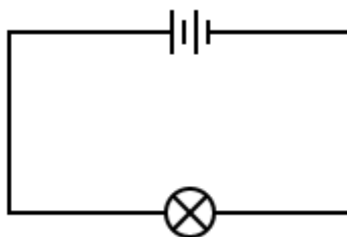


Fig. 1

On a copy of Fig.1, draw an ammeter and a voltmeter to show how these instruments can be connected in the circuit to measure the current through the lamp and the voltage across the lamp.

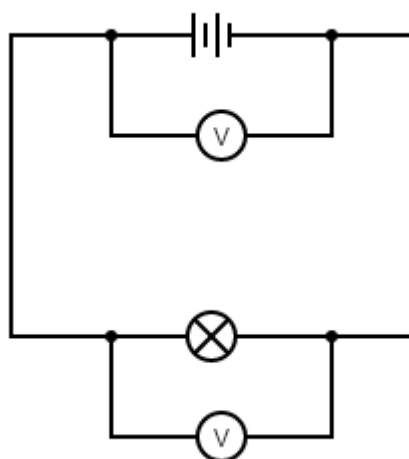2. Fig. 2 shows a battery connected to a lamp. Two voltmeters are also connected in the circuit as shown in the figure. The battery has a voltage of 6V.




A real battery has something called an internal resistance. Due to this internal resistance, when the battery supplies a current, the voltage across the battery will be less than the stated voltage of the battery. However, we ignore this internal resistance and its effect in GCSE physics.

Fig. 2

- (a) State the reading on the voltmeter connected across the battery.
  
- (b) State the reading on the voltmeter connected across the lamp.


3. Fig. 3 shows a 12V battery connected to a lamp of resistance  $24 \Omega$ .

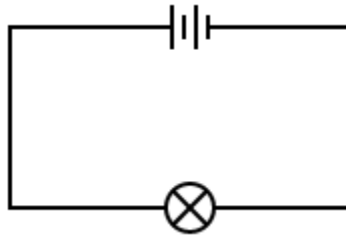

**Fig. 3**

- (a) State the voltage applied by the battery across the lamp.
- (b) Calculate the current flowing through the lamp.
- 

4. A battery is connected to an ammeter and a lamp as shown in fig.4.

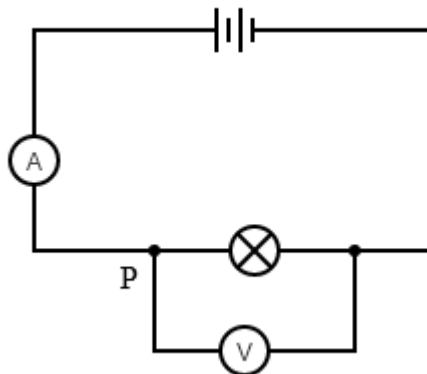

**Fig. 4**

The reading on the ammeter is 3A.

The reading on the voltmeter is 12V.

- (a) It is generally assumed that the current reaching junction P on Fig.4 doesn't split at that junction. Based on this, we say that the current flowing through the lamp is the same as the current reading on the ammeter.
- Why is this assumption justified?

- (b) Calculate the amount of charge passing through the lamp in 5 minutes.
- (c) Determine the number of electrons passing through the lamp in 5 minutes. (Each electron has a negative charge of  $1.6 \times 10^{-19}$  C of charge.)
- (d) Find the resistance of the lamp.
- 


5. In each of the following circuits, a resistor and a lamp are connected in series to a battery.

For each circuit, calculate the voltage (potential difference) across,


(i) the resistor

(ii) the lamp.


(a)

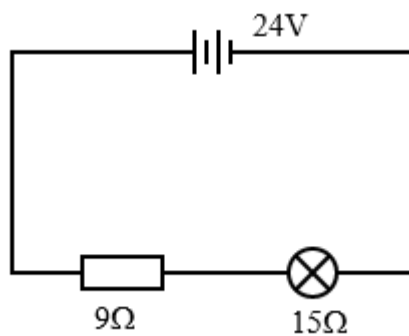

(b)

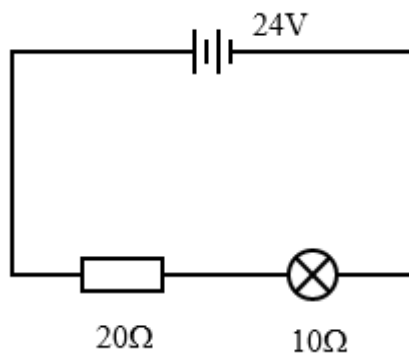

(c)

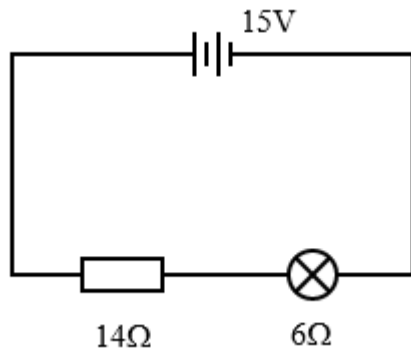


---

6. In each of the circuits in question 5 above, calculate the current flowing through the lamp.

---

7. Fig. 5 shows a battery of voltage 12V connected to a lamp and a resistor.

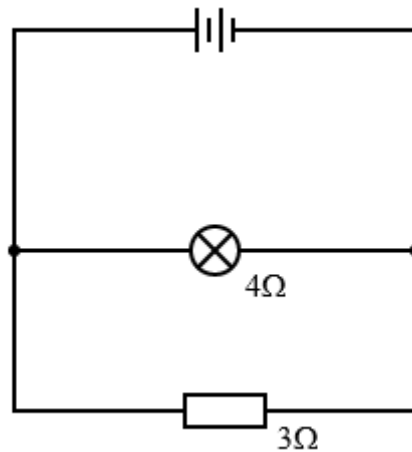

**Fig. 5**

State the voltage across the,

(i) lamp

(ii) resistor


---

8. In question 7 above, calculate the current flowing through the,


(i) lamp

(ii) resistor

9. Sam connects a 36V battery to two lamps and a resistor in two different ways as shown in Fig. 6 and Fig. 7.

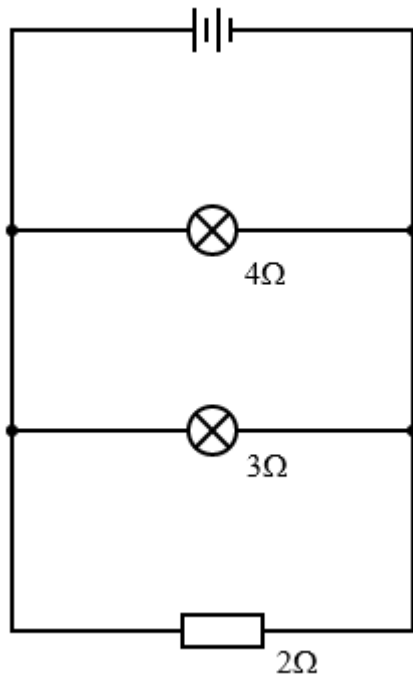


**Fig. 6**

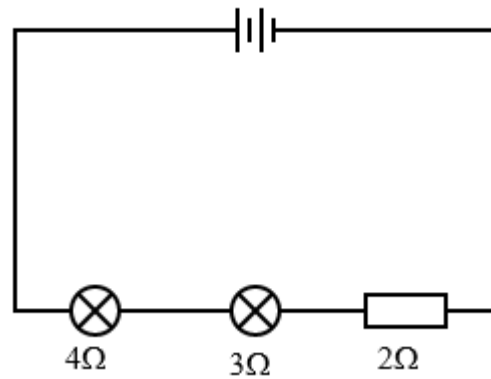


**Fig. 7**

- (a) For each circuit, determine the voltage across the,
- (i) 4Ω lamp
  - (ii) 3Ω lamp
  - (iii) resistor
- (b) Calculate the current through the 4Ω lamp in each of the circuits. Use your answer to state the circuit in which the 4Ω lamp will be brighter.
-

10. Fig. 8 and Fig 9 show a 24V battery connected to a lamp and a variable resistor in two different ways. The lamp has a fixed resistance of  $4\Omega$  .

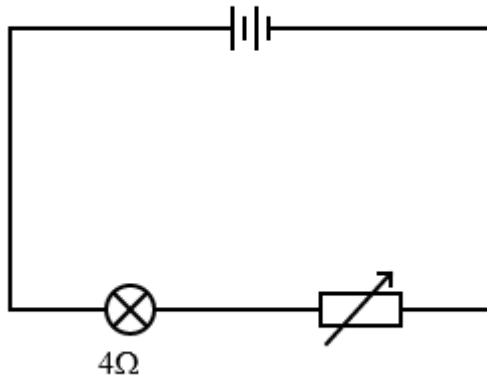

**Fig. 8**

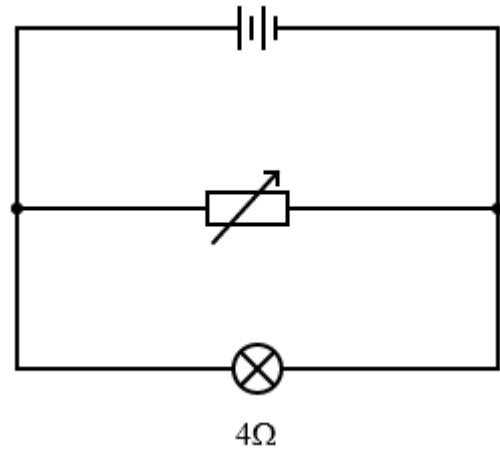

**Fig. 9**

- (a) The resistance of the variable resistor is set at  $8\Omega$  in both circuits.
- Calculate the potential differences across the lamp and the variable resistors in the two circuits.
  - Determine the current through the lamp in the circuits.
- (b) The resistance of the variable resistor is changed to  $12\Omega$  in both circuits. Without any calculations, state whether the brightness of the lamp will change in the two circuits.
-