

Exercise A

1.

$$\text{Charge } Q = CV = 20 \times 10^{-6} \text{ F} \times 6.0 \text{ V} = 120 \text{ } \mu\text{C}$$

$$\text{Energy} = \frac{1}{2}QV = \frac{1}{2} \times 120 \times 10^{-6} \text{ C} \times 6.0 \text{ V} = 360 \text{ } \mu\text{J}$$

When the voltage is doubled, the charge is doubled to 240 μC .

The energy stored is multiplied by 4, since both the charge and the voltage are doubled, to 1.44 mJ.

2.

$$F = C \text{ V}^{-1}$$

$$= C (\text{JC}^{-1})^{-1}$$

$$= C (\text{J}^{-1} \text{ C})$$

$$= C^2 \text{ J}^{-1}$$

3.

$$4.5 \text{ V}$$

4.

$$\text{(a) } 8.0 \text{ C;}$$

$$\text{(b) (i) } 8.0 \times 10^4 \text{ A; (ii) } 1.6 \text{ MW}$$

5.

$$\text{(a) } Q = CV = 0.00100 \text{ } \mu\text{F} \times 12 \text{ V} = 0.012 \text{ } \mu\text{C} \text{ (Note how the } \mu \text{ symbol can be carried through the equation.)}$$

$$\text{(b) (i) } \frac{1}{C} = \frac{1}{0.00100} + \frac{1}{0.000020} = 1000 + 50000 = 51000$$

$$C = \frac{1}{51000} = 1.96 \times 10^{-5} \text{ } \mu\text{F}$$

(ii) The charge Q on each capacitor and the total charge are the same, so

$$Q = CV = 12 \text{ V} \times 1.96 \times 10^{-5} \text{ } \mu\text{F} = 2.35 \times 10^{-4} \text{ } \mu\text{C}$$

(iii) The p.d. across the 0.00100 μF capacitor is

$$Q/C = 2.35 \times 10^{-4} \text{ } \mu\text{C} / 0.00100 \text{ } \mu\text{F} = 0.24 \text{ V. The p.d. across the } 0.000020 \text{ } \mu\text{F} \text{ capacitor is } Q/C = 2.35 \times 10^{-4} \text{ } \mu\text{C} / 0.000020 \text{ } \mu\text{F} = 11.76 \text{ V}$$

6.

- (a) (i) $3.0 \mu\text{F}$;
(ii) $180 \mu\text{C}$, $90 \mu\text{C}$, $90 \mu\text{C}$;
(iii) 30 V across each
(b) $9.0 \mu\text{F}$
(c) (i) $6.0 \mu\text{F}$: $240 \mu\text{C}$; $3.0 \mu\text{F}$: $60 \mu\text{C}$; $9.0 \mu\text{F}$: $180 \mu\text{C}$;
(ii) $6.0 \mu\text{F}$: 40 V ; $3.0 \mu\text{F}$: 20 V ; $9.0 \mu\text{F}$: 20 V
-

7.

- (a) (i) 15 mC ; (ii) 10 mC
(b) 10 V
(c) (i) 0.11 J ; (ii) 0.075 J
-

8.

The ratios are about 1.61 ± 0.05

9.

- (a) $CR = 22.2 \times 10^{-6} \times 90.1 \times 10^3 = 2.00 \text{ s}$
(These figures were arranged to make the time constant equal to 2.00 s .)

- (b) (i) $Q_0 = CV = 22.2 \times 10^{-6} \times 9.00 = 200 \mu\text{C}$
 $I_0 = -V_0/R = -9.00/90.1 \times 10^3 = -99.9 \mu\text{A}$
(the minus sign indicates discharge).

- (c) (i) $Q = Q_0 e^{-\frac{t}{CR}} = 200 \times 10^{-6} e^{-\frac{1.5}{2.0}} = 200 \times 10^{-6} e^{-0.75}$
 $= 200 \times 10^{-6} \times 0.472 = 94.5 \mu\text{C}$

- (ii) $I = I_0 e^{-\frac{t}{CR}} = -99.9 \times 10^{-6} e^{-\frac{1.5}{2.0}} = 99.9 \times 10^{-6} e^{-0.75}$
 $= 99.9 \times 10^{-6} \times 0.472 = 47.2 \mu\text{A}$

- (d) $Q = Q_0 e^{-\frac{CR}{CR}} = 200 \times 10^{-6} e^{-\frac{2.0}{2.0}} = 200 \times 10^{-6} e^{-1.0}$
 $= 200 \times 10^{-6} \times 0.368 = 73.6 \mu\text{C}$

The charge remaining on any capacitor after one time constant is always 36.8% of the charge at time $t = 0$.

10.

- (a) 0.65 mA ;
(b) (i) 6.5 V ; (ii) 0.16 mA ;
(c) (i) 9.6 V ; (ii) 0.24 mA ;
(e) 26 s .
-

Exercise B

1.

- a** i $Q_0 = CV_0 = 2200 \times 10^{-6} \times 9.0 = 2.0 \times 10^{-2} \text{ C}.$
ii Time constant $= RC = 100 \times 10^3 \times 2.2 \times 10^{-3} = 220 \text{ s}.$
b i When $t = RC$, $V = V_0 e^{-1} = 0.37 \times 9.0 = 3.3 \text{ V}.$
ii When $t = 300 \text{ s}$, $\frac{t}{RC} = \frac{300}{220} = 1.36$
Therefore, $V = V_0 e^{-\frac{t}{RC}} = 9.0 e^{-1.36} = 2.3 \text{ V}.$
-

2.

- a** i $300 \mu\text{C}$
ii 5.0 s
b i 5 s approx
ii $20 \text{ k}\Omega$
-

3.

- a** i 0.61 mC
ii 0.45 mA
b $0.23 \text{ V}, 11 \mu\text{A}$
-

4.

- a** $13 \mu\text{C}, 40 \mu\text{J}$
b $0.62 \text{ V}, 0.42 \mu\text{J}$
-

5.

- a** i 60 mA
ii 0.34 mJ
b 1.4 s
c 0.32 mJ
-

6.

- a** i C increases
ii Q increases
b The energy stored $= \frac{1}{2} QV$, so the energy stored increases because Q increases and V is unchanged.
-

7.

a 9.8 pF

b 1100 pJ

