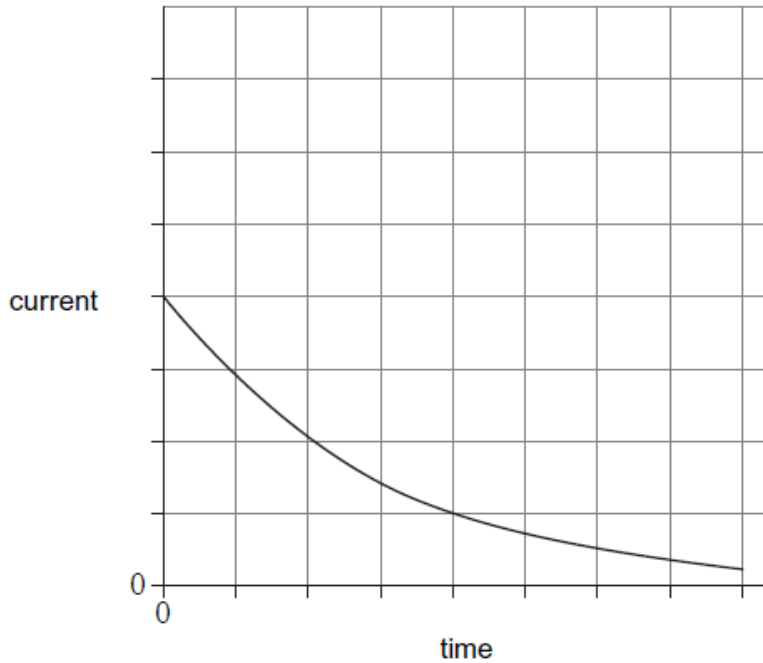


Mixed Exam Questions – Set 9

1.

- (a) Figure 4 shows how the current varies with time as a capacitor is discharged through a 150Ω resistor.

Figure 4



- (a) (i) Explain how the initial charge on the capacitor could be determined from a graph of current against time.

[1 mark]

.....

.....

.....

.....

- (a) (ii) The same capacitor is charged to the same initial potential difference (pd) and then discharged through a $300 \text{ k}\Omega$ resistor. Sketch a second graph on the same axes above to show how the current varies with time in this case.

[3 marks]

- (b) In an experiment to show that a capacitor stores energy, a student charges a capacitor from a battery and then discharges it through a small electric motor. The motor is used to lift a mass vertically.
- (b) (i) The capacitance of the capacitor is 0.12 F and it is charged to a pd of 9.0 V. The weight of the mass raised is 3.5 N. Calculate the maximum height to which the mass could be raised. Give your answer to an appropriate number of significant figures.

[4 marks]

maximum height m

- (b) (ii) Give two reasons why the value you have calculated in part (b)(i) would not be achieved in practice.

[2 marks]

- 1
-
-
-
-
- 2
-
-
-

2.

(a) When an uncharged capacitor is charged by a **constant** current of $4.5\ \mu\text{A}$ for $60\ \text{s}$ the pd across it becomes $4.4\ \text{V}$.


(a) (i) Calculate the capacitance of the capacitor.

[3 marks]

capacitance F

(a) (ii) The capacitor is charged using the circuit shown in **Figure 5**. The battery emf is $6.0\ \text{V}$ and its internal resistance is negligible. In order to keep the current constant at $4.5\ \mu\text{A}$, the resistance of the variable resistor R is decreased steadily as the charge on the capacitor increases.

Figure 5

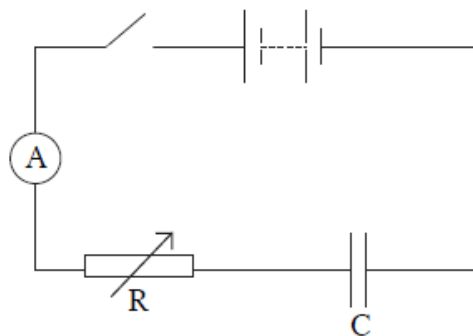


Calculate the resistance of R when the uncharged capacitor has been charging for $30\ \text{s}$.

[3 marks]

resistance Ω

- (b) The circuit in **Figure 6** contains a cell, an uncharged capacitor, a fixed resistor and a two-way switch.

Figure 6

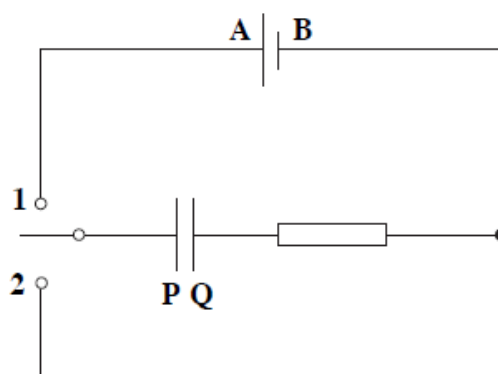

The switch is moved to position **1** until the capacitor is fully charged. The switch is then moved to position **2**.

Describe what happens in this circuit after the switch is moved to position **1**, and after it has been moved to position **2**. In your answer you should refer to:

- the direction in which electrons flow in the circuit, and how the flow of electrons changes with time,
- how the potential differences across the resistor and the capacitor change with time,
- the energy changes which take place in the circuit.

The terminals of the cell are labelled **A** and **B** and the capacitor plates are labelled **P** and **Q** so that you can refer to them in your answer.

The quality of your written communication will be assessed in your answer.

[6 marks]

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

3.

(a)


State what is meant by a capacitance of $370 \mu\text{F}$

[2 marks]

(b)

The charging of a $370 \mu\text{F}$ capacitor is investigated using the circuit shown in **Figure 4**. Both meters in the circuit are ideal.

Figure 4

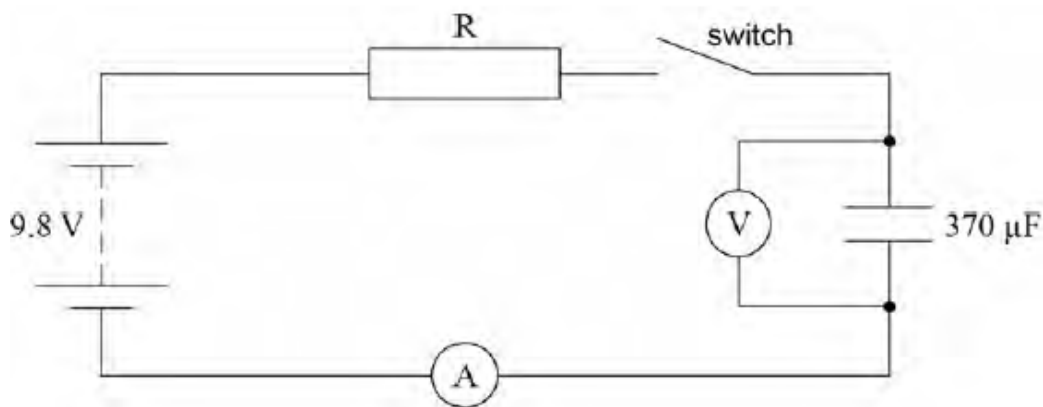

The power supply of emf 9.8 V has a negligible internal resistance. The capacitor is initially uncharged. When the switch is closed at time $t = 0$ charge begins to flow through resistor R. The time constant of the charging circuit is 1.0 s

Calculate the resistance of R.

[1 mark]

resistance of R = _____ Ω


(c)

Identify, with the symbol X on **Figure 5**, the potential difference (pd) across the capacitor when the switch has been closed for 2.0 s

Sketch the graph that shows how the pd varies from $t = 0$ to $t = 2.0$ s

[2 marks]

Figure 5

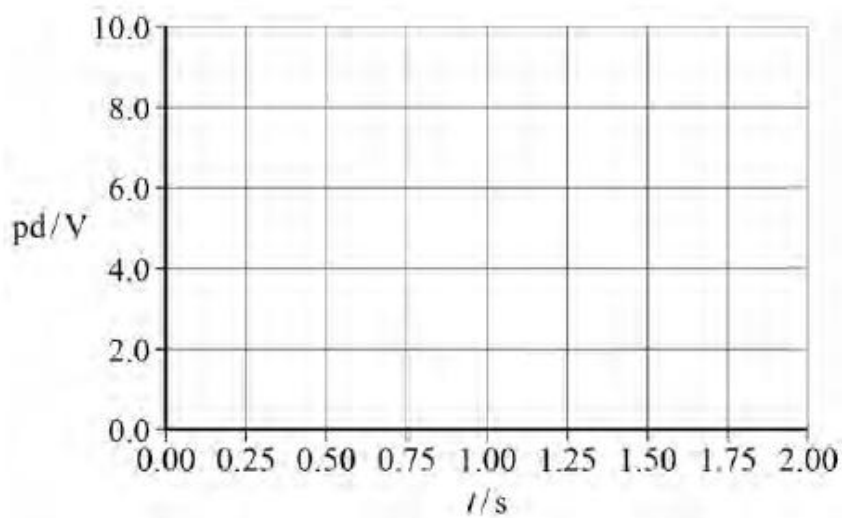

(d)

Calculate the time taken for the charging current to fall to half its initial value.

[1 mark]

time = _____ s

(e)

Calculate the time taken for the charge on the capacitor to reach 3.0 mC

[3 marks]

time = _____ s

Question 4 is on the next page.

4.

(a) Define *capacitance*.

.....
..... [1]

(b) Fig. 1.1 shows a circuit consisting of a resistor and a capacitor of capacitance $4.5\mu\text{F}$.

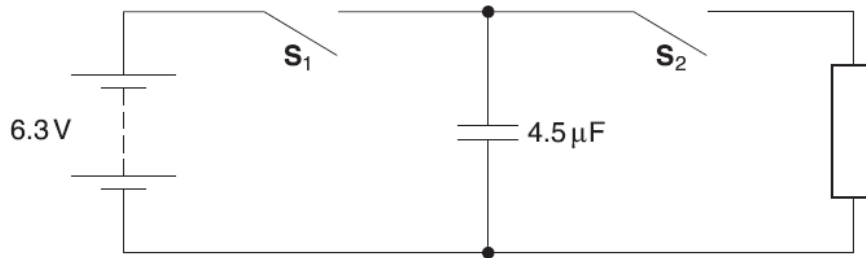


Fig. 1.1

Switch S_1 is closed and switch S_2 is left open. The potential difference across the capacitor is 6.3V.

Calculate

(i) the charge stored by the capacitor

charge = μC [1]

(ii) the energy stored by the capacitor.

energy = J [2]

(c) Switch S_1 is opened and switch S_2 is closed.

(i) Describe and explain in terms of the movement of electrons how the potential difference across the capacitor changes.

.....

..... [3]

(ii) The energy stored in the capacitor decreases to zero. State where the initial energy stored in the capacitor is dissipated.

.....

..... [1]

(d) Fig.1.2 shows the $4.5\mu\text{F}$ capacitor now connected in parallel with a capacitor of capacitance $1.5\mu\text{F}$. Both switches are open and both capacitors are uncharged.

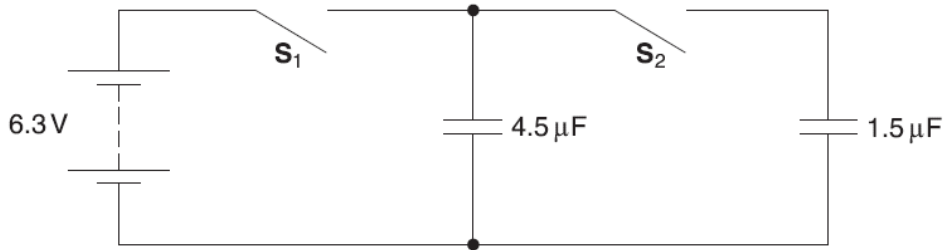


Fig. 1.2

Switch S_1 is closed. The potential difference across the $4.5\mu\text{F}$ capacitor is now 6.3V. Switch S_1 is opened and then switch S_2 is closed.

(i) Calculate the total capacitance of the circuit when S_2 is closed.

capacitance = μF [1]

(ii) Calculate the final potential difference across the capacitors.

potential difference = V [2]

5.

(a) Define *capacitance*.

.....
..... [1]

(b) Fig. 2.1 shows two capacitors of capacitance $150\ \mu\text{F}$ and $450\ \mu\text{F}$ connected in series with a battery of e.m.f. 6.0V . The battery has negligible internal resistance.

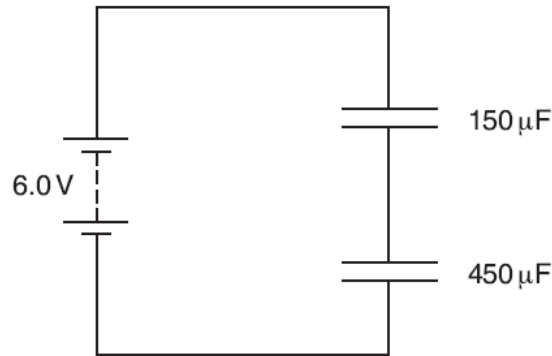


Fig. 2.1

For the circuit shown in Fig. 2.1, calculate

(i) the potential difference across the $150\ \mu\text{F}$ capacitor

potential difference = V [2]

(ii) the charge stored by the $150\ \mu\text{F}$ capacitor

charge = C [1]

(iii) the total capacitance of the circuit.

capacitance = F [1]

- (c) The fully charged capacitors shown in (b) are disconnected from the battery. The capacitors are then connected in series with a resistor R of resistance $45\text{k}\Omega$ and an open switch S as shown in Fig. 2.2.

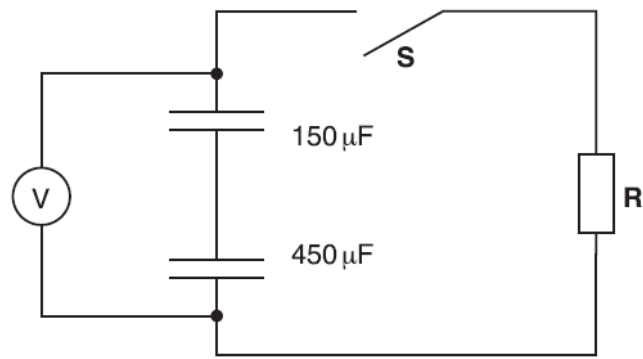


Fig. 2.2

The p.d. V across the capacitors is measured with a voltmeter of infinite resistance. The switch S is closed at time $t = 0$ and measurements of V are made at regular time intervals.

- (i) Show that the time constant for the circuit is about 5 s.

[1]

- (ii) On Fig. 2.3 sketch the variation of p.d. V with time t .

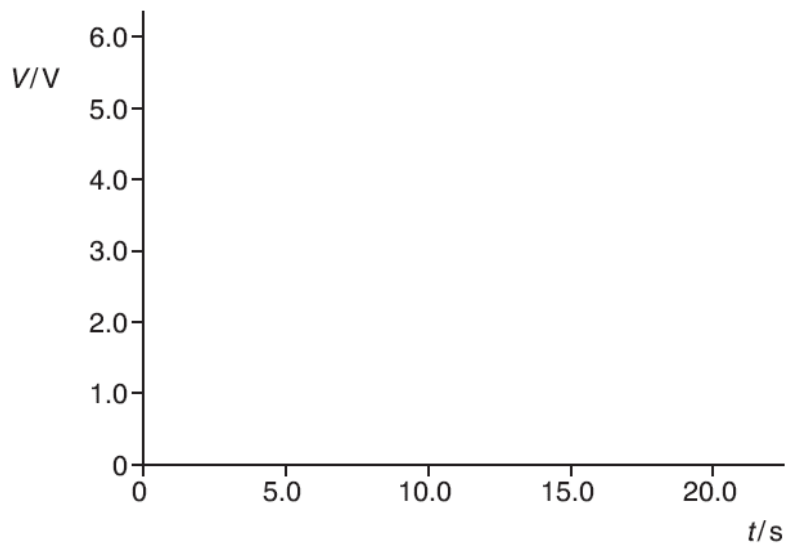


Fig. 2.3

[3]

(iii) At time $t = 0$ calculate the ratio

$$\frac{\text{energy stored by the } 150\ \mu\text{F capacitor}}{\text{energy stored by the } 450\ \mu\text{F capacitor}}$$

ratio = [2]

(iv) State and explain how the ratio varies with time.

.....
.....
..... [2]
